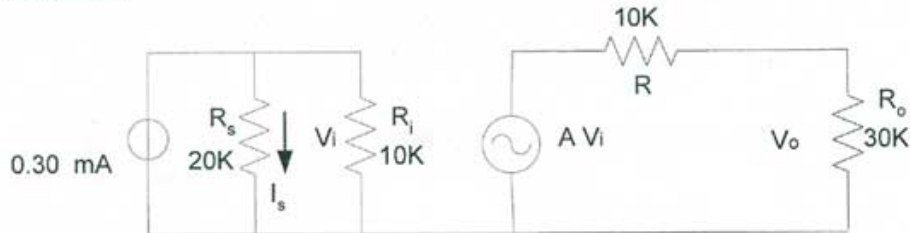


| | | |
|---|--|------------------------------------|
| February 11, 2004 Duration: 50 minutes | EE311 Midterm Exam. # 1 (Closed notes & book) | Spring 2004 School of EECS/ WSU |
| Name: _____ | | ID #: _____ |

Problem 1:



In the above amplifier circuit, $A=800$. Determine the following:

a) Voltage gain $A_v = V_o/V_i = A V_i \frac{R_o}{R+R_o} = 800 \times \frac{30}{40}$ $A_v = 600 \text{ V/V}$

$$V_o = \frac{30}{30+10} A V_i \Rightarrow \frac{V_o}{V_i} = \frac{30}{40} \times 800$$

b) Current gain $A_i = I_o/I_i = \frac{V_o/R_o}{V_i/R_i} = \frac{V_o}{V_i} \times \frac{R_i}{R_o} = 600 \times \frac{10}{30}$ $A_i = 200 \text{ A/A}$


c) Current gain $A_{is} = I_o/I_s$

$$I_s = V_i/R_s$$

$$A_{is} = 400 \text{ A/A}$$

$$\frac{I_o}{I_s} = \frac{V_o/R_o}{V_i/R_s} = \left(\frac{V_o}{V_i}\right) \cdot \left(\frac{R_s}{R_o}\right) = 600 \cdot \frac{20}{30}$$

Problem 2:

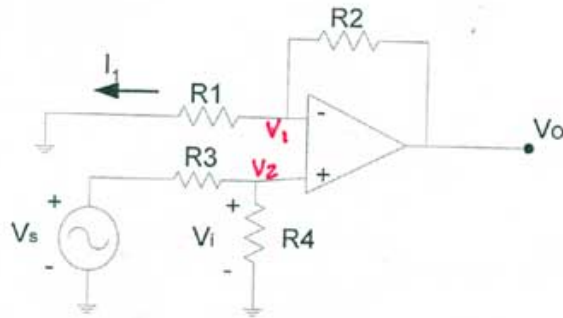

In the OpAmp circuits, $R1 = 1K$, $R2 = 199 K$, $R3 = 40K$, and $R4 = 10K$. Assuming the OpAmp is ideal, Determine the following:

a) Voltage gain $A_v = V_o / V_i$ $V_2 = V_i$ $A_v = \underline{200 \text{ V/V}}$

$$A_v = \frac{V_o}{V_i} = (1 + R_2/R_1)$$

b) Over all voltage gain $A_{vs} = V_o / V_s$ $V_o = (1 + R_2/R_1) V_i$ $A_{vs} = \underline{40 \text{ V/V}}$

$$V_i = \frac{R_4 V_s}{R_3 + R_4} = \frac{1}{1 + R_3/R_4} V_s$$


$$\frac{V_o}{V_s} = \frac{(1 + R_2/R_1)}{(1 + R_3/R_4)} = \frac{200}{1 + 4} = 40$$

c) If $V_s = 50 \text{ mV}$, determine the current through $R1$. $V_1 = V_2$ $I_1 = \underline{10 \mu A}$

$$V_2 = V_i = \frac{V_s}{1 + 4} = \frac{50 \text{ mV}}{5} = 10 \text{ mV}$$

$$I_1 = \frac{10 \text{ mV}}{10^3} = \frac{10^{-2}}{10^3} = 10^{-5} \text{ A} = \underline{10 \times 10^{-6}}$$

Problem 3

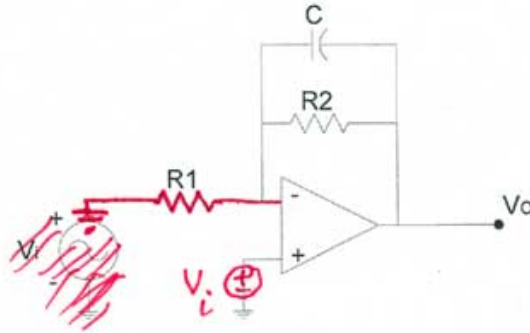

In the above amplifier circuit, $R_2 = 100\text{K}$, $C = 1\text{ nF}$, and the cutoff frequency $\omega_T = 500\text{ kHz}$.rad
Determine the following:

a) The 3 dB frequency $\omega_{3dB} = \underline{10\text{ kHz}}$

$$1 + \frac{Z_2}{R_1} = 1 + \frac{1}{R_1(1/R_2 + j\omega C)} = 1 + \frac{R_2/R_1}{1 + j\omega R_2 C}$$

R_1 unknown, Assume $\omega_{3dB} = \frac{1}{R_2 C} = \frac{1}{10^5 \times 10^{-9}} = \underline{10\text{ kHz}}$

b) The low frequency amplifier gain $A_v = \underline{50}$

$$A_v(\omega \rightarrow 0) = 1 + R_2/R_1 = 50$$

$$A_v \omega_{3dB} = 1 \cdot \omega_T \quad A_v = \frac{500\text{ kHz}}{10\text{ kHz}}$$


c) Value of resistance R_1 $R_1 = \underline{2.04\text{ k}\Omega}$

$$50 = 1 + R_2/R_1$$

$$R_2/R_1 = 49 \Rightarrow R_1 = \frac{R_2}{49} = \frac{100}{49}$$

$$\begin{array}{r} 2.04 \\ 49 \overline{) 100} \\ \underline{98} \\ 200 \end{array}$$

Problem 5:

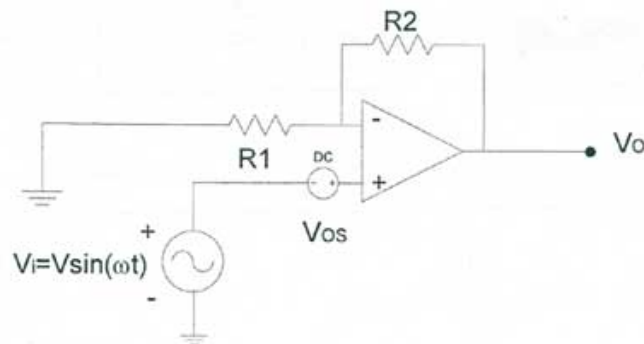

The above OpAmp has slew rate = $10V/\mu s$ and offset voltage $V_{os} = 10\text{ mV}$, $R_1 = 1\text{K}\Omega$, $R_2 = 99\text{K}\Omega$. If the magnitude of maximum output swing = 10V .

a) Determine the maximum amplitude of input signal V_i

$$V = \underline{90\text{ mV}}$$

$$\text{max } V_i = V$$

$$A_v = 1 + R_2/R_1 = 100$$

$$V_o = A_v(V_i + V_{os})$$

$$100V_i + 1\text{V} = 10\text{V}, \quad V_i = \frac{9\text{V}}{100}$$

c) If the input signal angular frequency $\omega = 1\text{ MHz rad}$, what the maximum amplitude of the input signal?

$$\left. \frac{dV_o}{dt} \right|_{\text{max}} = A_v \left. \frac{dV_i}{dt} \right|_{\text{max}} = A_v V \omega = SR$$

$$V = \frac{10}{100 \times 10^6 \times 10^6}$$

$$= \underline{\underline{100\text{ mV}}}$$

d) What is the useful input voltage range?

Maximum useful range is limited by $V_o \Rightarrow 90\text{ mV}$