

HW 4 Solution

Problem 2.36 Use the Smith chart to find the normalized load impedance corresponding to a reflection coefficient:

- (a) $\Gamma = 0.5$,
- (b) $\Gamma = 0.5 \angle 60^\circ$,
- (c) $\Gamma = -1$,
- (d) $\Gamma = 0.3 \angle -30^\circ$,
- (e) $\Gamma = 0$,
- (f) $\Gamma = j$.

Solution: Refer to Fig. P2.36.

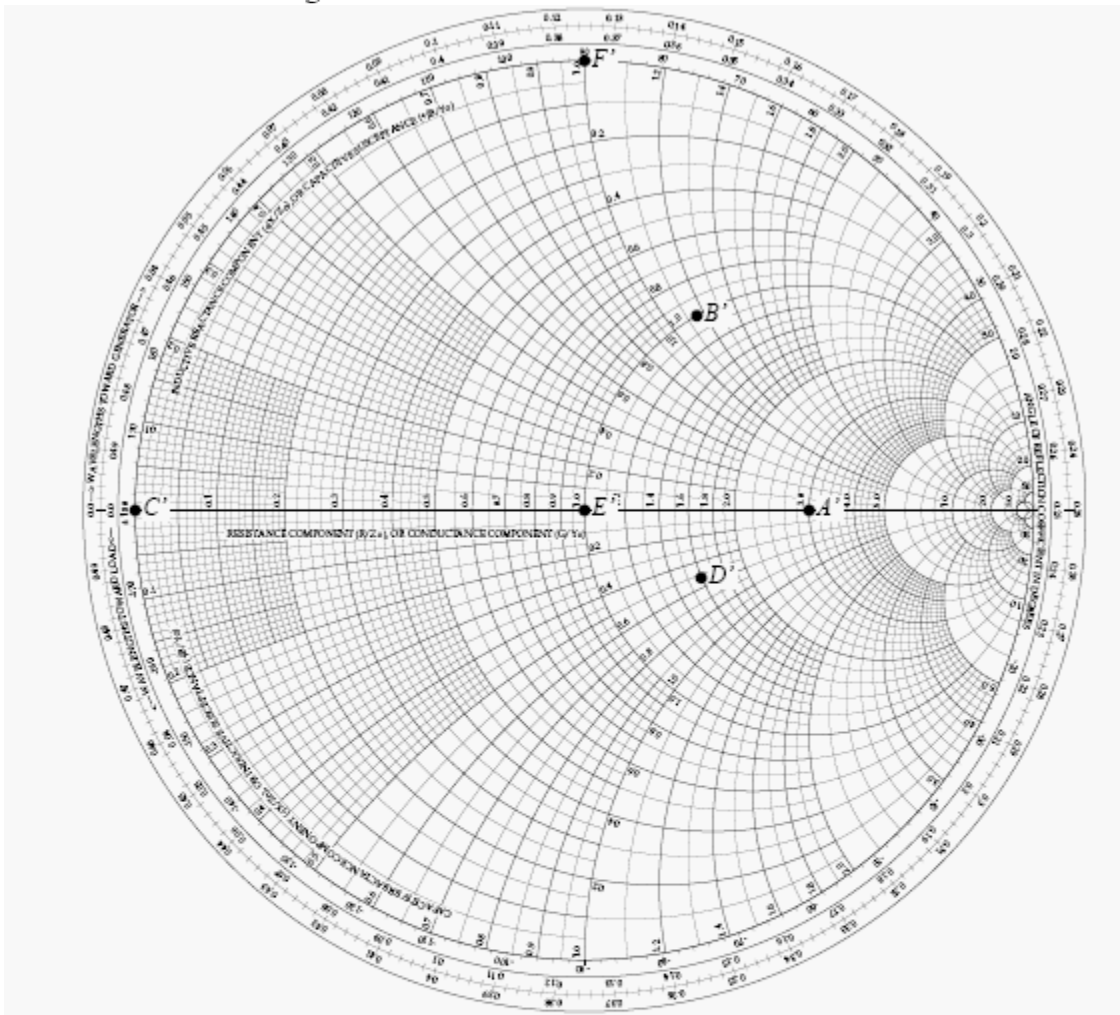


Figure P2.36: Solution of Problem 2.36.

- (a) Point A' is $\Gamma = 0.5$ at $z_L = 3 + j0$.
- (b) Point B' is $\Gamma = 0.5e^{j60^\circ}$ at $z_L = 1 + j1.15$.
- (c) Point C' is $\Gamma = -1$ at $z_L = 0 + j0$.
- (d) Point D' is $\Gamma = 0.3e^{-j30^\circ}$ at $z_L = 1.60 - j0.53$.
- (e) Point E' is $\Gamma = 0$ at $z_L = 1 + j0$.
- (f) Point F' is $\Gamma = j$ at $z_L = 0 + j1$.

Problem 2.38 A lossless $50\text{-}\Omega$ transmission line is terminated in a load with $Z_L = (50 - j25)\text{ }\Omega$. Use the Smith chart to find the following:

- the reflection coefficient Γ ,
- the standing-wave ratio,
- the input impedance at 0.35λ from the load,
- the input admittance at 0.35λ from the load,
- the shortest line length for which the input impedance is purely resistive,
- the position of the first voltage maximum from the load.

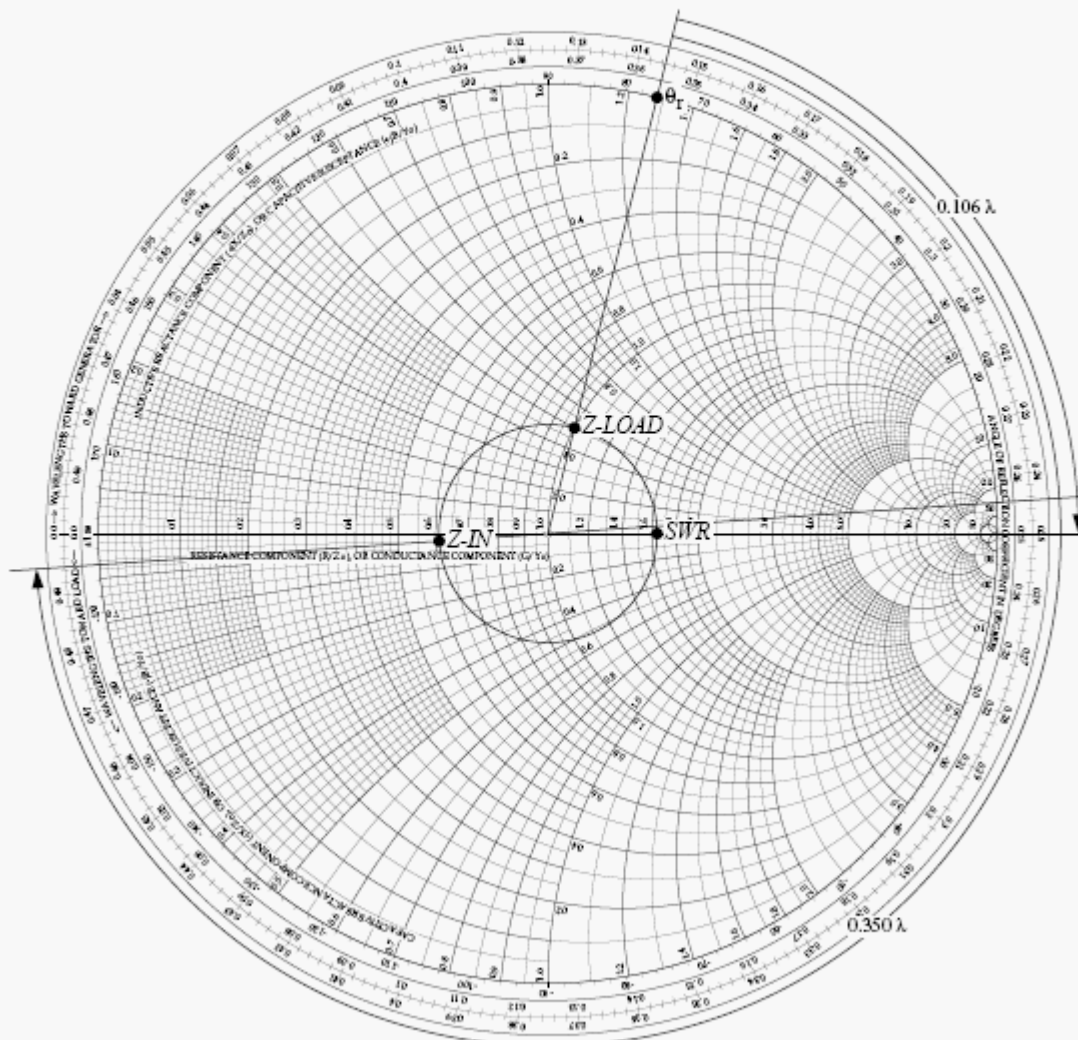


Figure P2.38: Solution of Problem 2.38.

Solution: Refer to Fig. P2.38. The normalized impedance

$$z_L = \frac{(50 - j25) \Omega}{50 \Omega} = 1 - j0.5$$

is at point *Z-LOAD*.

(a) $\Gamma = 0.24e^{j76.0^\circ}$ The angle of the reflection coefficient is read of that scale at the point θ_r .

(b) At the point *SWR*: $S = 1.64$.

(c) Z_{in} is 0.350λ from the load, which is at 0.144λ on the wavelengths to generator scale. So point *Z-IN* is at $0.144\lambda + 0.350\lambda = 0.494\lambda$ on the WTG scale. At point *Z-IN*:

$$Z_{in} = z_{in}Z_0 = (0.61 - j0.022) \times 50 \Omega = (30.5 - j1.09) \Omega.$$

(d) At the point on the SWR circle opposite *Z-IN*,


$$Y_{in} = \frac{y_{in}}{Z_0} = \frac{(1.64 - j0.06)}{50 \Omega} = (32.7 - j1.17) \text{ mS}.$$

(e) Traveling from the point *Z-LOAD* in the direction of the generator (clockwise), the SWR circle crosses the $x_L = 0$ line first at the point *SWR*. To travel from *Z-LOAD* to *SWR* one must travel $0.250\lambda - 0.144\lambda = 0.106\lambda$. (Readings are on the wavelengths to generator scale.) So the shortest line length would be 0.106λ .

(f) The voltage max occurs at point *SWR*. From the previous part, this occurs at $z = -0.106\lambda$.

Problem 2.40 Use the Smith chart to find y_L if $z_L = 1.5 - j0.7$.

Solution: Refer to Fig. P2.40. The point Z represents $1.5 - j0.7$. The reciprocal of point Z is at point Y , which is at $0.55 + j0.26$.

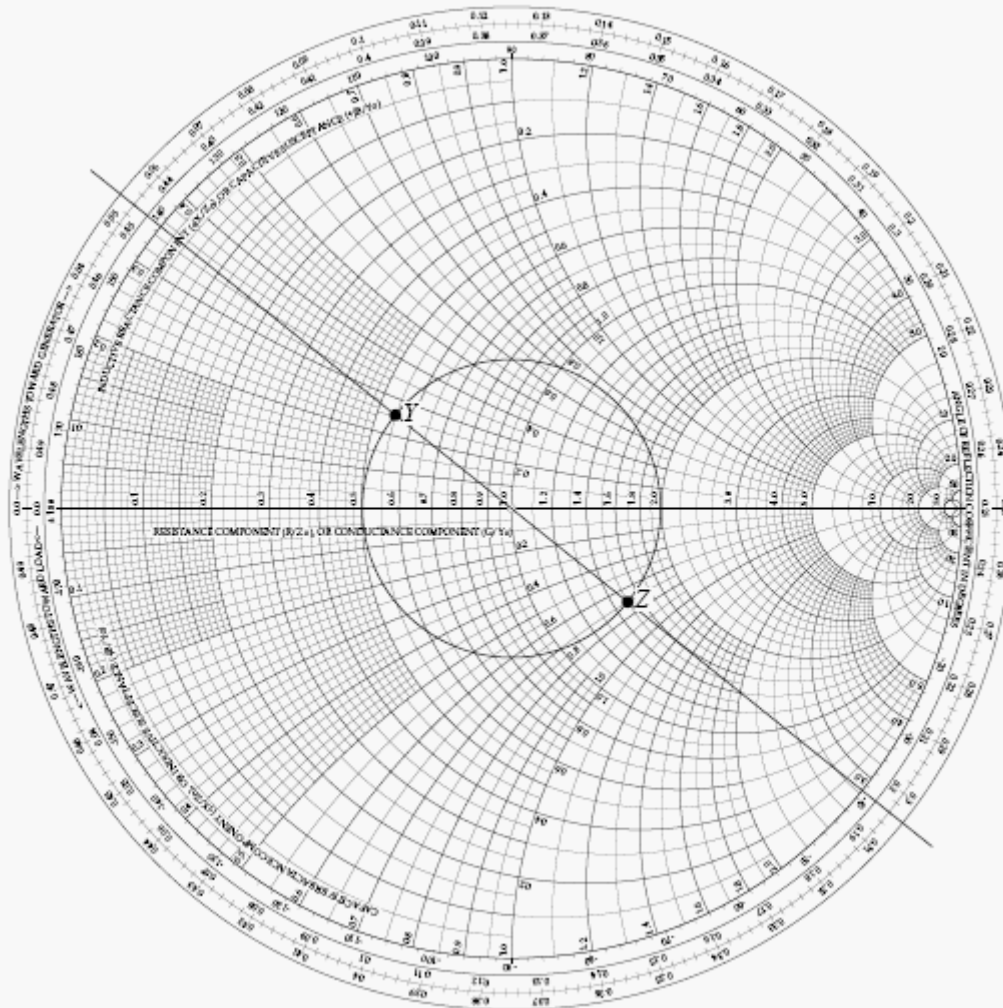

Problem 2.41 A lossless $100\text{-}\Omega$ transmission line $3\lambda/8$ in length is terminated in an unknown impedance. If the input impedance is $Z_{\text{in}} = -j2.5\ \Omega$,

(a) use the Smith chart to find Z_L .

(b) What length of open-circuit line could be used to replace Z_L ?

Solution: Refer to Fig. P2.41. $z_{\text{in}} = Z_{\text{in}}/Z_0 = -j2.5\ \Omega/100\ \Omega = 0.0 - j0.025$ which is at point *Z-IN* and is at 0.004λ on the wavelengths to load scale.

(a) Point *Z-LOAD* is 0.375λ toward the load from the end of the line. Thus, on the wavelength to load scale, it is at $0.004\lambda + 0.375\lambda = 0.379\lambda$.

$$Z_L = z_L Z_0 = (0 + j0.95) \times 100\ \Omega = j95\ \Omega.$$

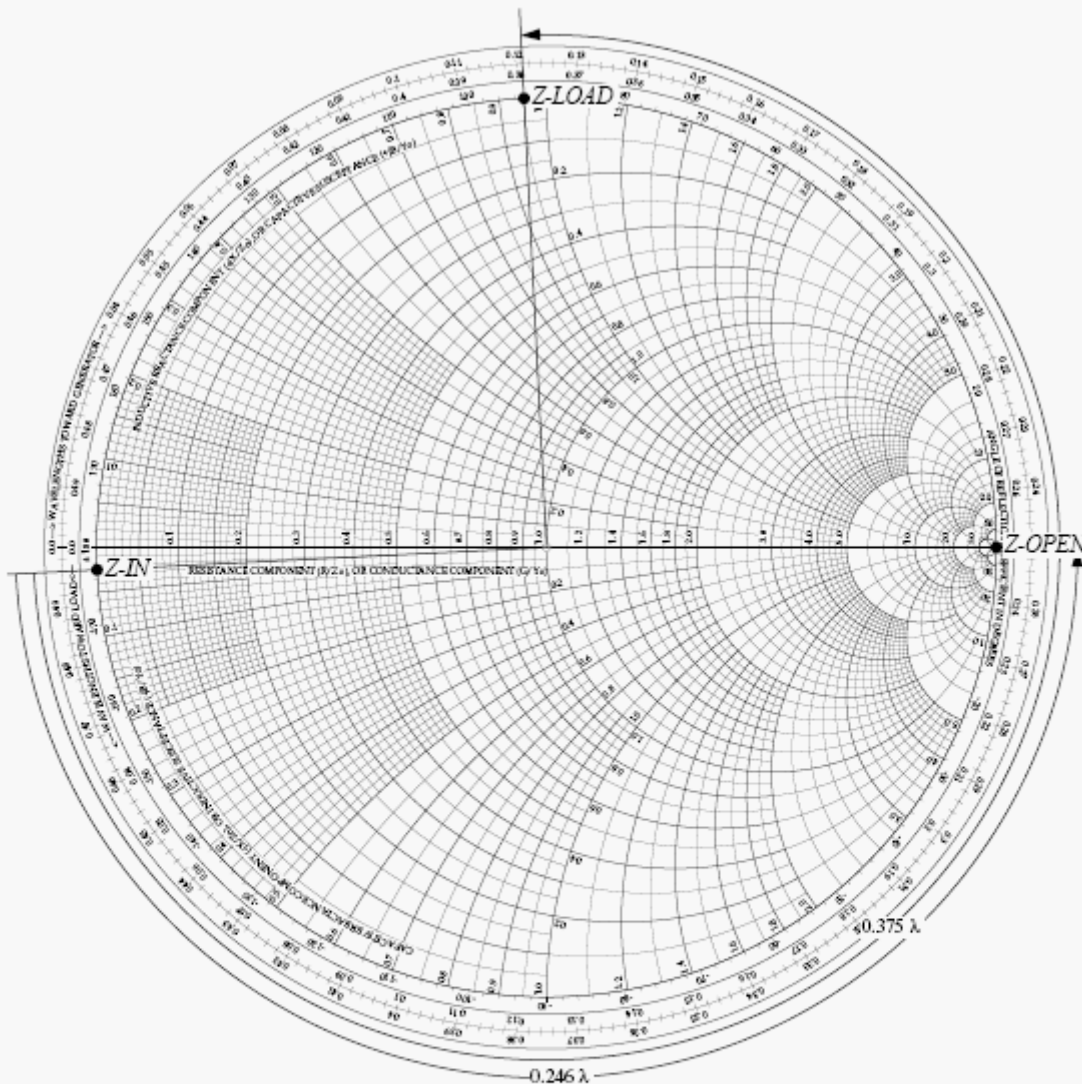


Figure P2.41: Solution of Problem 2.41.

(b) An open circuit is located at point *Z-OPEN*, which is at 0.250λ on the wavelength to load scale. Therefore, an open circuited line with $Z_{\text{in}} = j0.025$ must have a length of $0.250\lambda - 0.004\lambda = 0.246\lambda$.